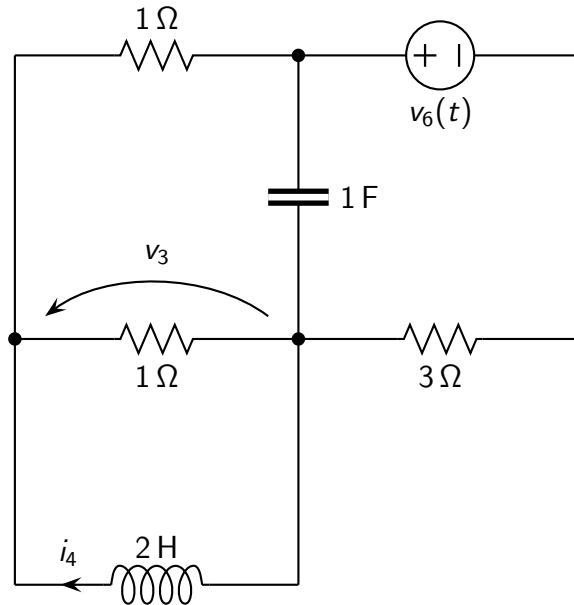


Problem: the circuit operates at steady-state. Find the expression of $v_3(t)$, $i_4(t)$.

Data: $v_6(t) = \cos(3t + 150^\circ) \text{ V}$.



Solution

$$v_3(t) = 54.019 \cos(3 t + 81^\circ) \text{ mV}$$

$$i_4(t) = 9.003 \cos(3 t + 171^\circ) \text{ mA}$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.