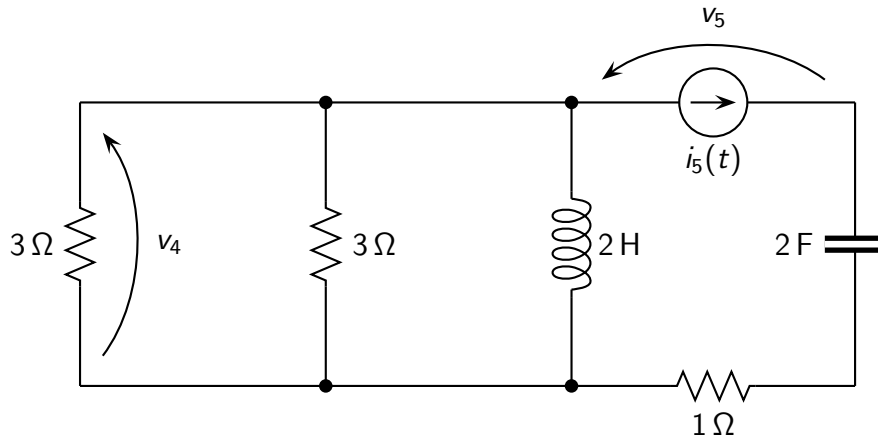


Problem: the circuit operates at steady-state. Find the expression of $v_4(t)$, $v_5(t)$.

Data: $i_5(t) = 3 \sin(t - 105^\circ)$ A.



Solution

$$v_4(t) = 3.6 \cos(t + 22^\circ) \text{ V}$$

$$v_5(t) = 5.917 \cos(t - 9^\circ) \text{ V}$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).