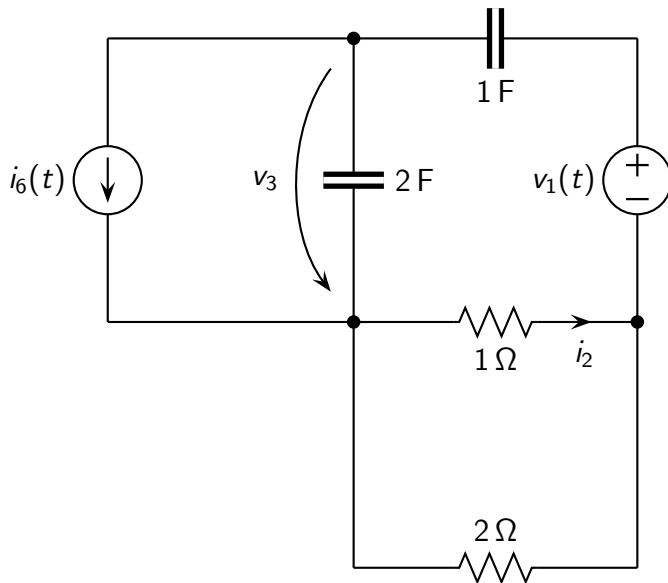


Problem: the circuit operates at steady-state. Find the expression of $i_2(t)$, $v_3(t)$.


Data: $v_1(t) = \sin(2t + 135^\circ) \text{ V}$, $i_6(t) = 3 \cos(2t - 45^\circ) \text{ A}$.



Solution

$$i_2(t) = 0.166 \cos(2 t + 93^\circ) \text{ A}$$
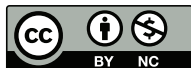
$$v_3(t) = 0.798 \cos(2 t - 138^\circ) \text{ V}$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.