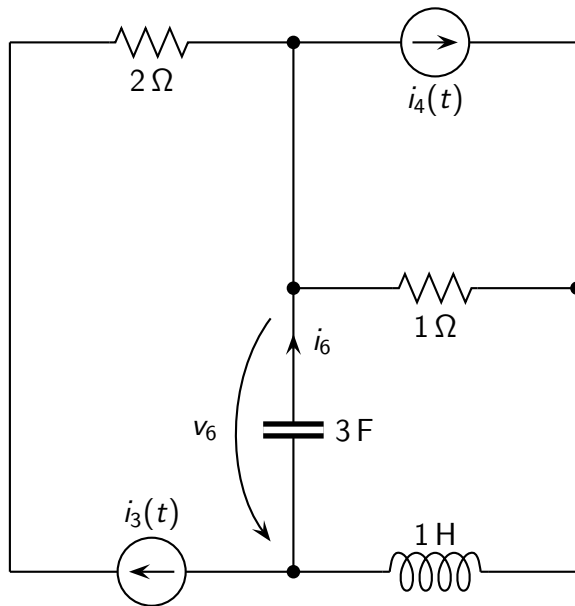


Problem: the circuit operates at steady-state. Find the expression of $v_6(t)$, $i_6(t)$.

Data: $i_3(t) = \cos(2t + 120^\circ)$ A, $i_4(t) = \cos(2t - 120^\circ)$ A.



Solution

$$v_6(t) = 0.15 \cos(2t - 174^\circ) \text{ V}$$

$$i_6(t) = 0.9 \cos(2t - 84^\circ) \text{ A}$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.