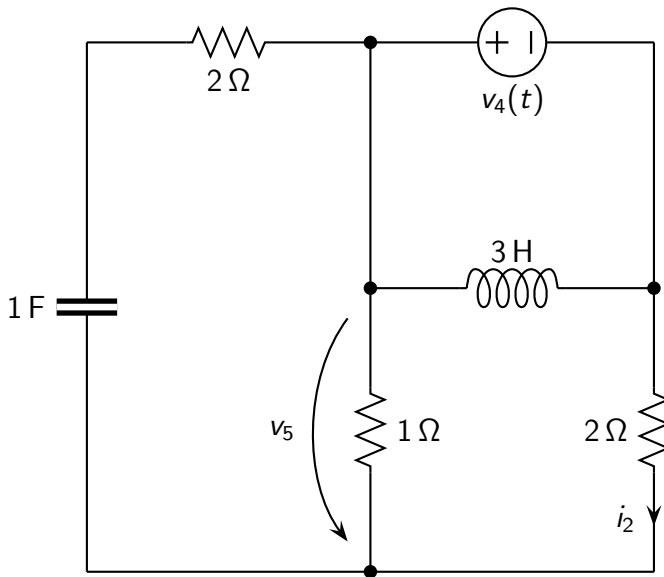


Problem: the circuit operates at steady-state. Find the expression of $i_2(t)$, $v_5(t)$.

Data: $v_4(t) = 2 \cos(2t + 15^\circ) \text{ V}$.



Solution

$$i_2(t) = 0.747 \cos(2 t - 164^\circ) \text{ A}$$

$$v_5(t) = 0.507 \cos(2 t - 168^\circ) \text{ V}$$

