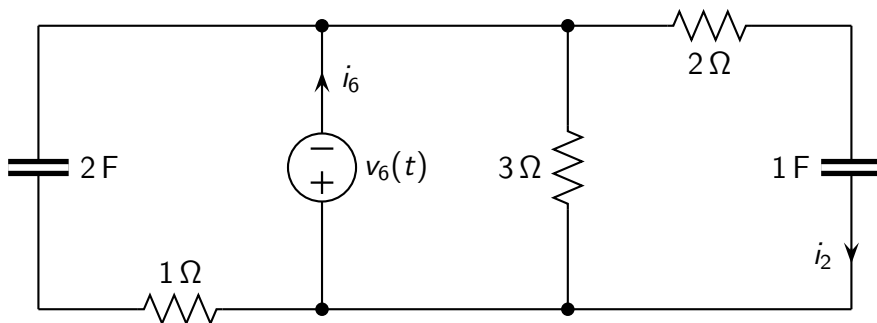


Problem: the circuit operates at steady-state. Find the expression of $i_6(t)$, $i_2(t)$.

Data: $v_6(t) = \cos(t - 165^\circ)$ V.



Solution

$$i_6(t) = 1.647 \cos(t + 36^\circ) \text{ A}$$

$$i_2(t) = 0.447 \cos(t + 42^\circ) \text{ A}$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).