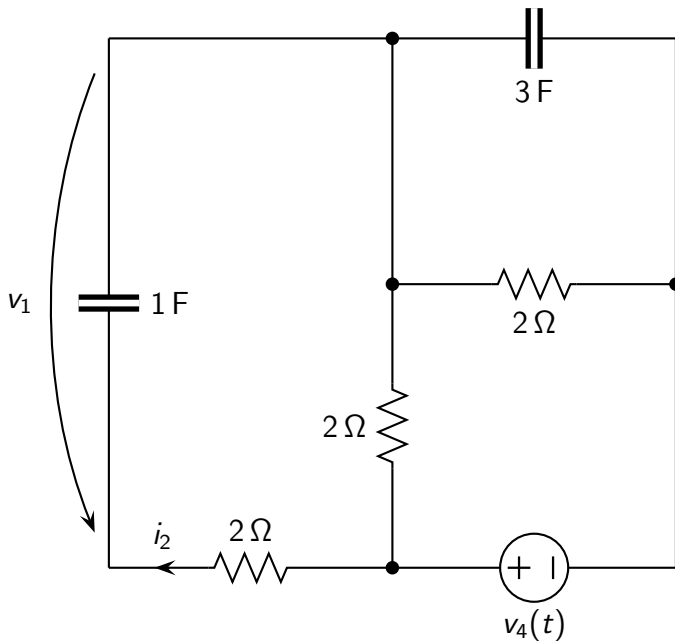


Problem: the circuit operates at steady-state. Find the expression of $v_1(t)$, $i_2(t)$.

Data: $v_4(t) = 3 \sin(t + 15^\circ) \text{ V}$.



Solution

$$v_1(t) = 1.168 \cos(t - 124^\circ) \text{ V}$$

$$i_2(t) = 1.168 \cos(t - 34^\circ) \text{ A}$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.