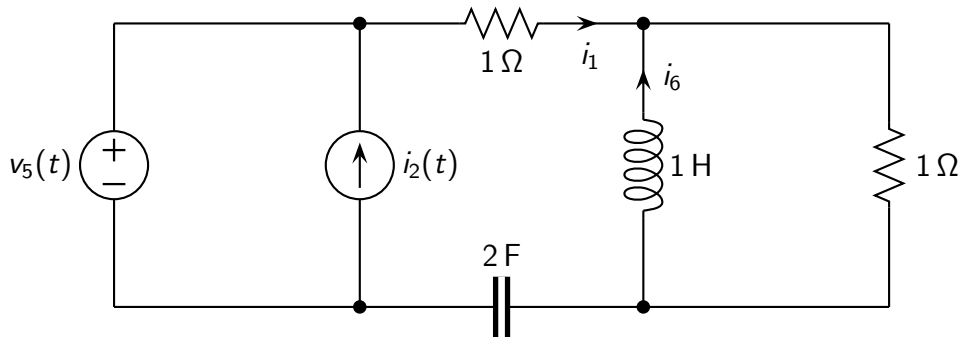


Problem: the circuit operates at steady-state. Find the expression of $i_1(t)$, $i_6(t)$.

Data: $i_2(t) = \sin(2t + 165^\circ)$ A, $v_5(t) = 2 \cos(2t + 15^\circ)$ V.



Solution

$$i_1(t) = 1.107 \cos(2 t + 10^\circ) \text{ A}$$

$$i_6(t) = 0.495 \cos(2 t + 127^\circ) \text{ A}$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).