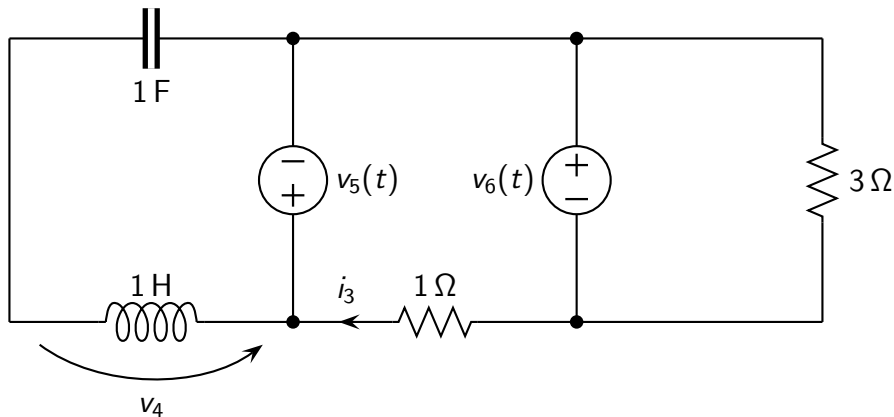


Problem: the circuit operates at steady-state. Find the expression of $i_3(t)$, $v_4(t)$.

Data: $v_5(t) = \sin(2t)$ V, $v_6(t) = 2 \sin(2t + 180^\circ)$ V.



Solution

$$i_3(t) = \cos(2t - 90^\circ) \text{ A}$$

$$v_4(t) = 1.333 \cos(2t - 90^\circ) \text{ V}$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).