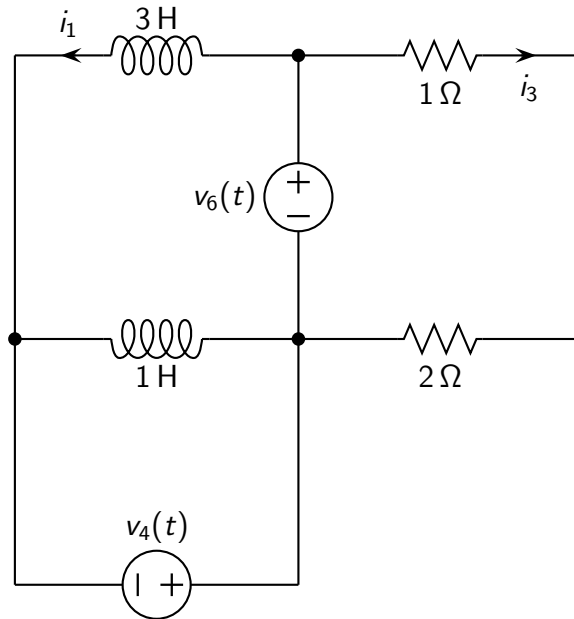


Problem: the circuit operates at steady-state. Find the expression of $i_1(t)$, $i_3(t)$.

Data: $v_4(t) = 3 \cos(t - 135^\circ) \text{ V}$, $v_6(t) = 3 \cos(t + 30^\circ) \text{ V}$.



Solution

$$i_1(t) = 0.261 \cos(t - 143^\circ) \text{ A}$$

$$i_3(t) = \cos(t + 30^\circ) \text{ A}$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.