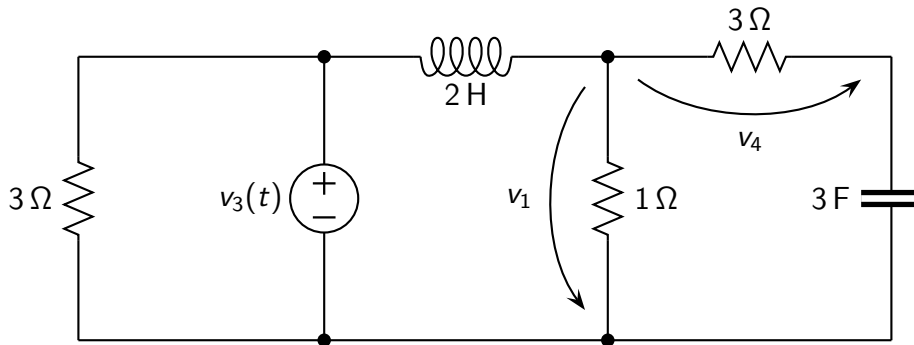


Problem: the circuit operates at steady-state. Find the expression of $v_1(t)$, $v_4(t)$.

Data: $v_3(t) = 3 \cos(3t + 165^\circ) \text{ V}$.



Solution

$$v_1(t) = 0.373 \cos(3t - 98^\circ) \text{ V}$$

$$v_4(t) = 0.372 \cos(3t - 96^\circ) \text{ V}$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).