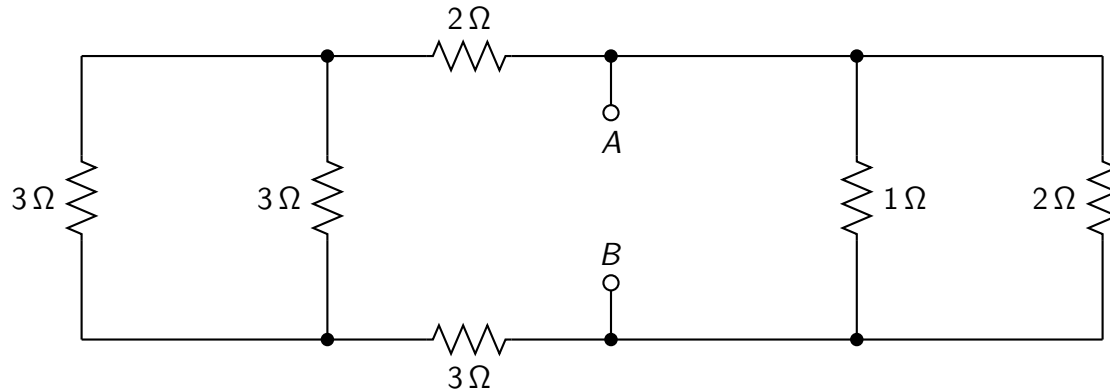


Problem: find the equivalent resistance R_{eq} between terminals A and B .



Solution

$$R_{eq} = \frac{26}{43} \Omega$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).