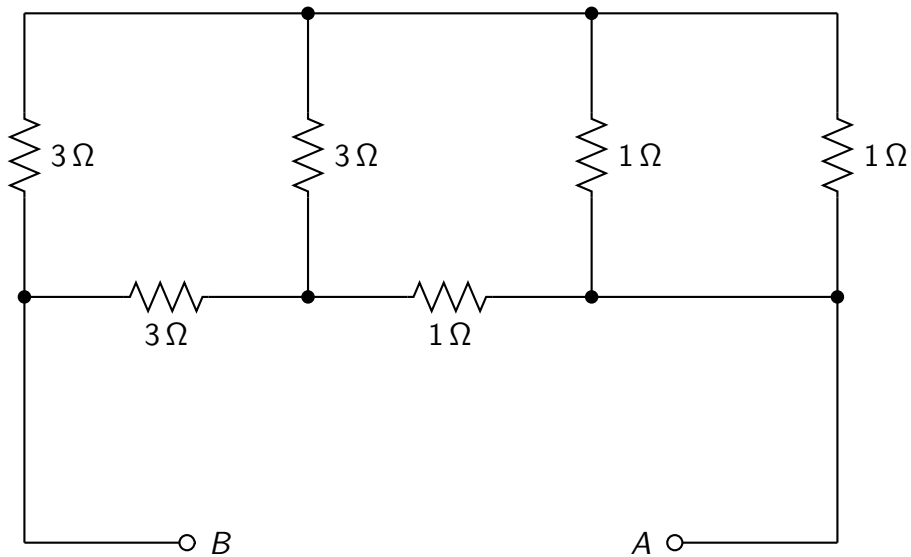


Problem: find the equivalent resistance R_{eq} between terminals A and B .



Solution

$$R_{eq} = \frac{13}{7} \Omega$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.