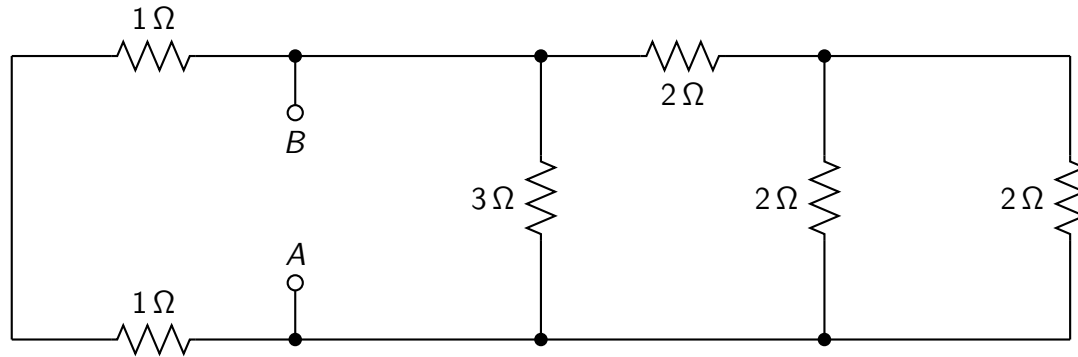


**Problem:** find the equivalent resistance  $R_{eq}$  between terminals  $A$  and  $B$ .



## Solution

$$R_{eq} = \frac{6}{7} \Omega$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).