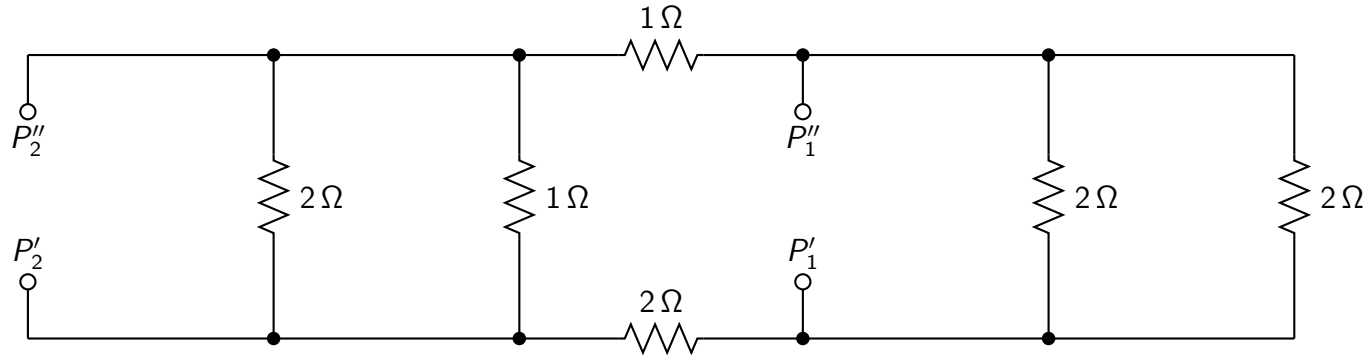


Problem: find the Resistance matrix of the two-port.



Solution

$$\mathbf{R} = \begin{pmatrix} \frac{11}{14} & \frac{1}{7} \\ \frac{1}{7} & \frac{4}{7} \end{pmatrix} \Omega$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).