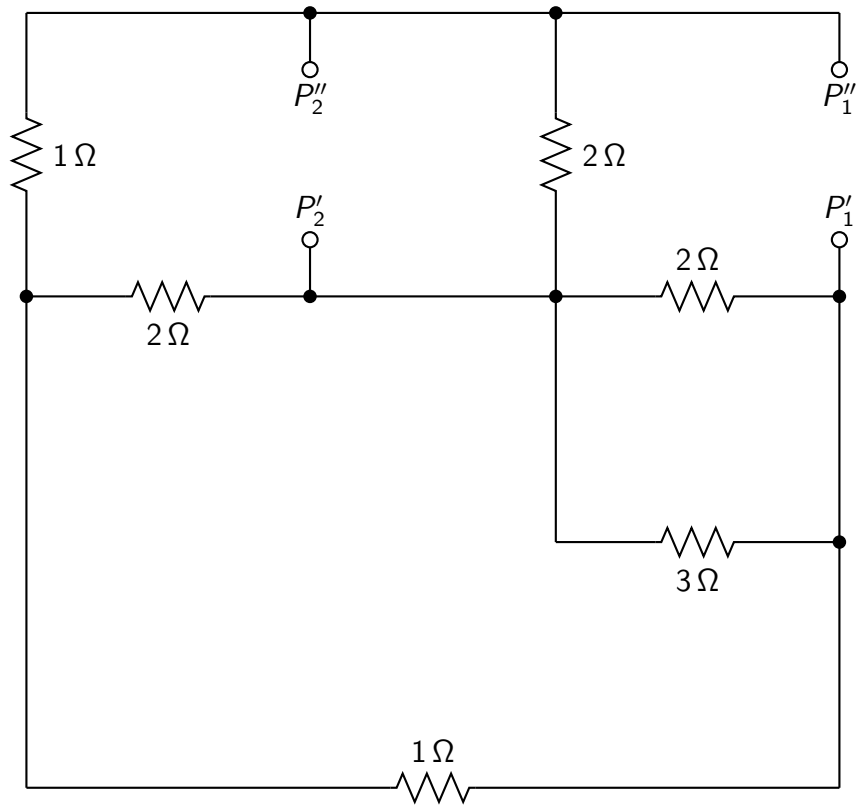


Problem: find the Conductance matrix of the two-port.



Solution

$$\mathbf{G} = \begin{pmatrix} \frac{43}{30} & \frac{-31}{30} \\ \frac{-31}{30} & \frac{26}{15} \end{pmatrix} \mathbf{S}$$