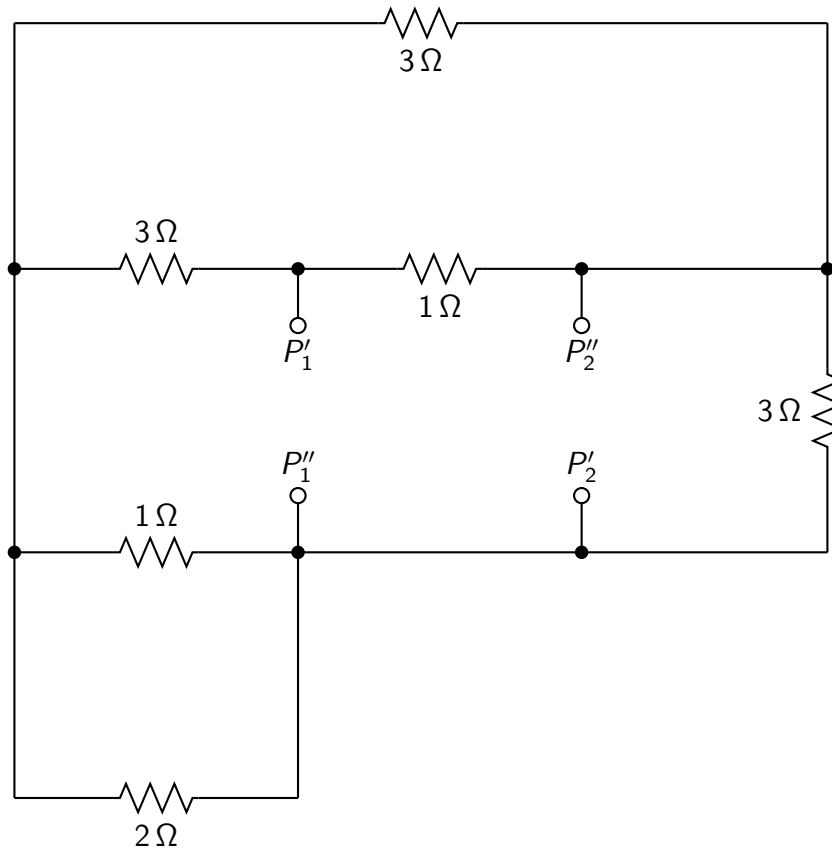


Problem: find the Resistance matrix of the two-port.



Solution

$$\mathbf{R} = \begin{pmatrix} 1.673 & -1.088 \\ -1.088 & 1.327 \end{pmatrix} \Omega$$