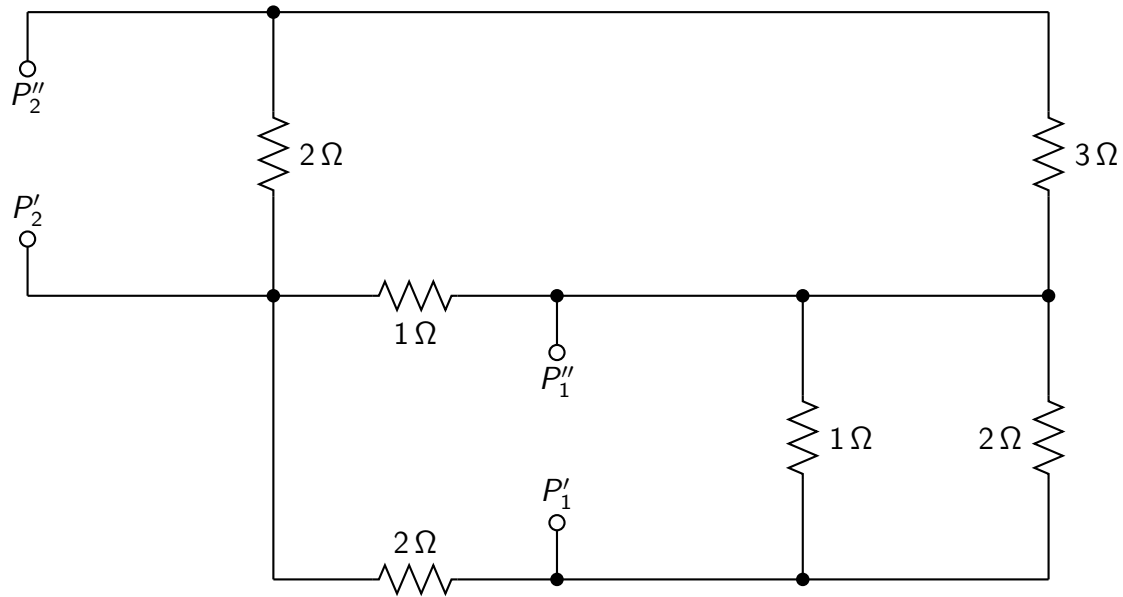


Problem: find the Hybrid-1 matrix of the two-port.



Solution

$$\mathbf{h} = \begin{pmatrix} \frac{22}{41} & \frac{2}{41} \\ \frac{-2}{41} & \frac{63}{82} \end{pmatrix}$$

