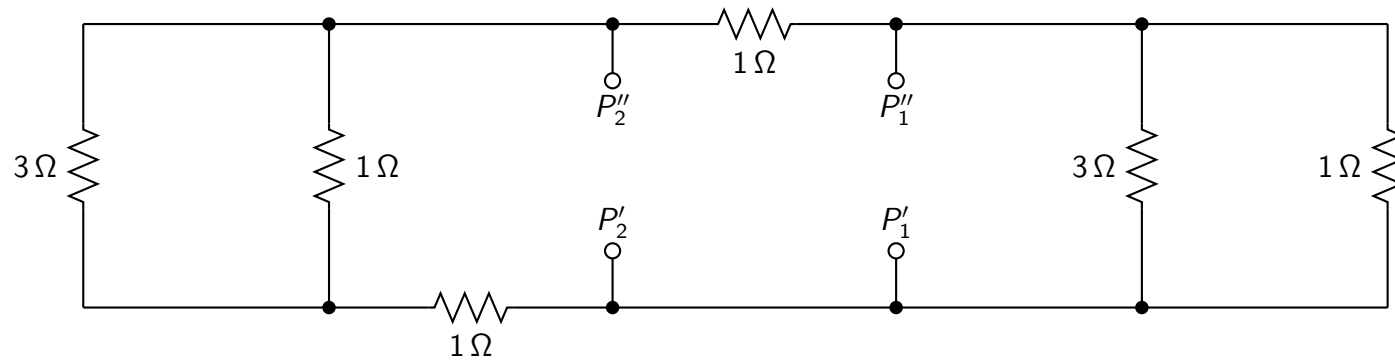


Problem: find the Conductance matrix of the two-port.



Solution

$$\mathbf{G} = \begin{pmatrix} \frac{7}{3} & -1 \\ -1 & \frac{11}{7} \end{pmatrix} \mathbf{S}$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).