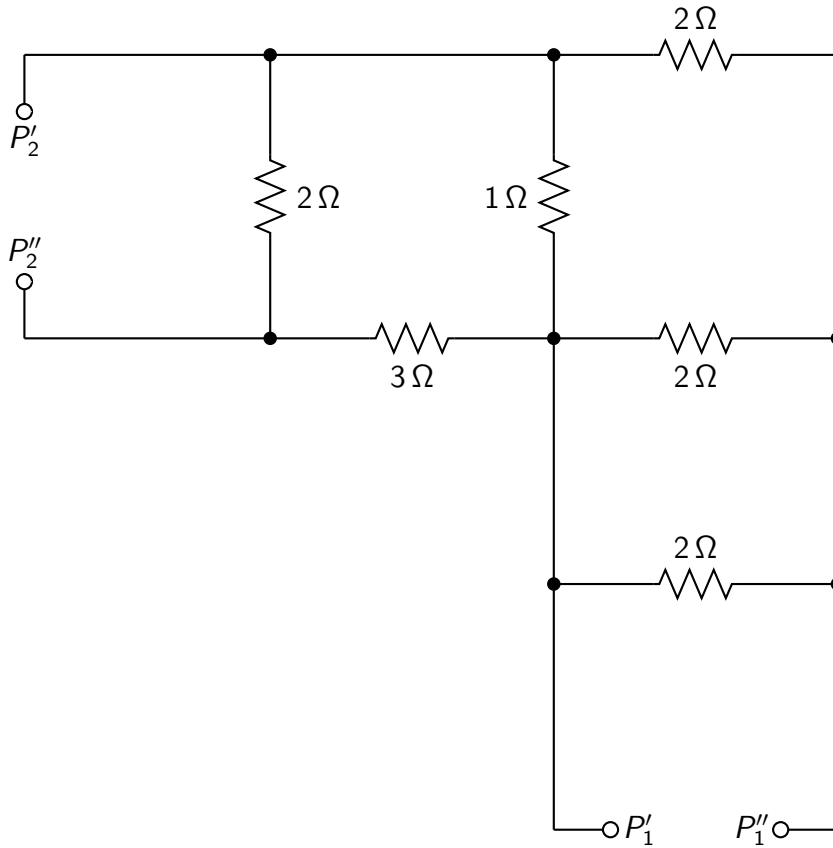


Problem: find the Hybrid-2 matrix of the two-port.



Solution

$$\mathbf{g} = \begin{pmatrix} \frac{23}{17} & \frac{2}{17} \\ -\frac{2}{17} & \frac{22}{17} \end{pmatrix}$$