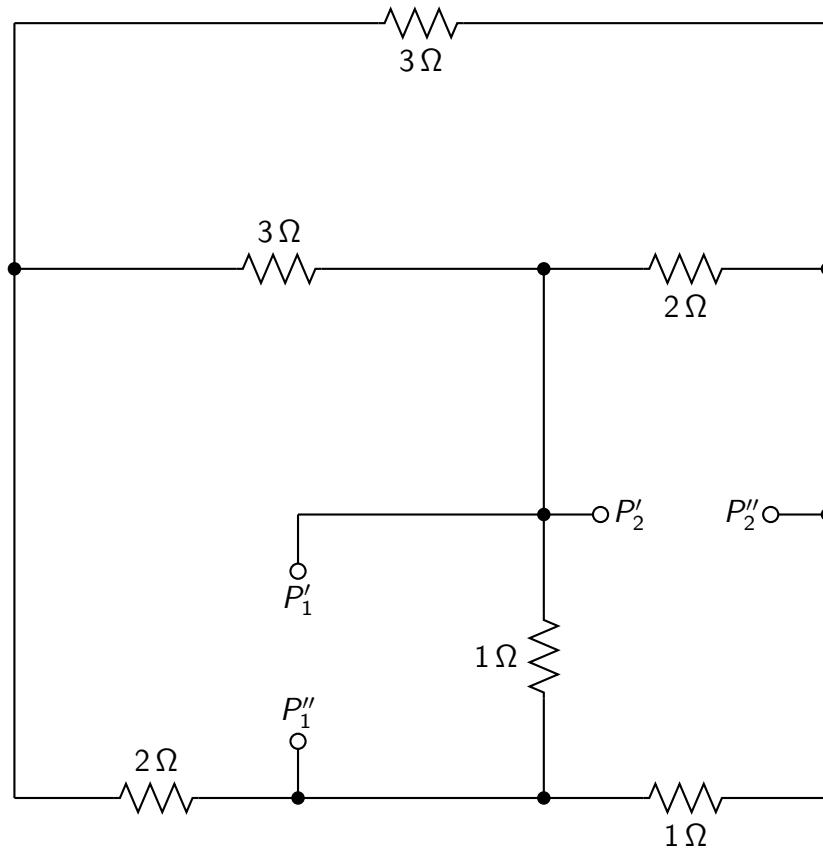


Problem: find the Hybrid-1 matrix of the two-port.



Solution

$$\mathbf{h} = \begin{pmatrix} \frac{7}{16} & \frac{1}{2} \\ \frac{-1}{2} & \frac{7}{6} \end{pmatrix}$$