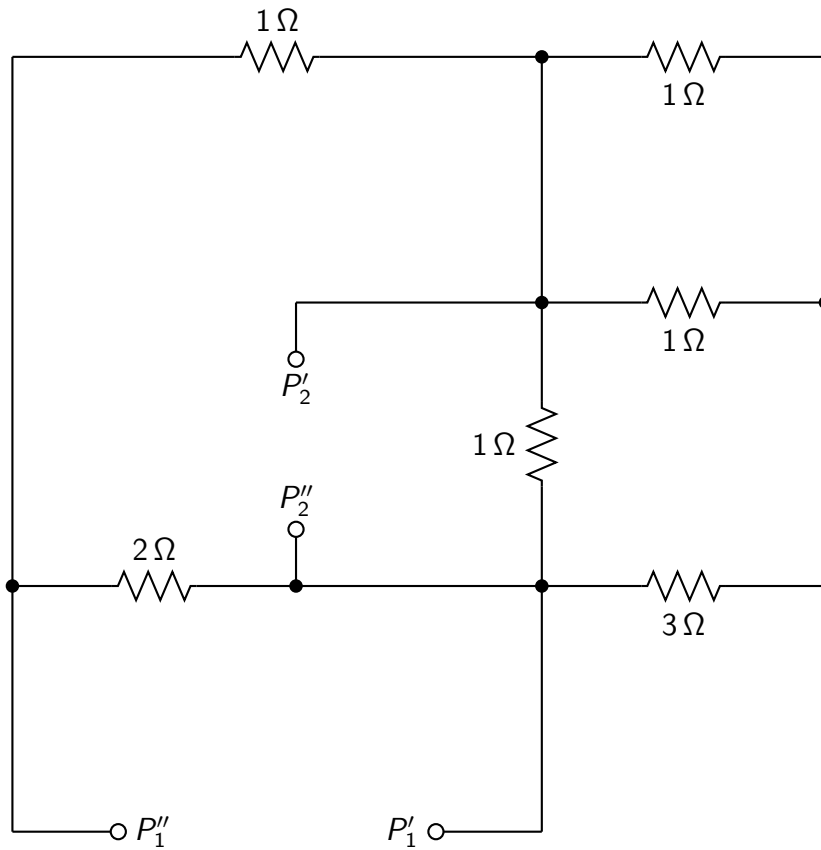


Problem: find the Conductance matrix of the two-port.



Solution

$$\mathbf{G} = \begin{pmatrix} \frac{3}{2} & 1 \\ 1 & \frac{16}{7} \end{pmatrix} S$$