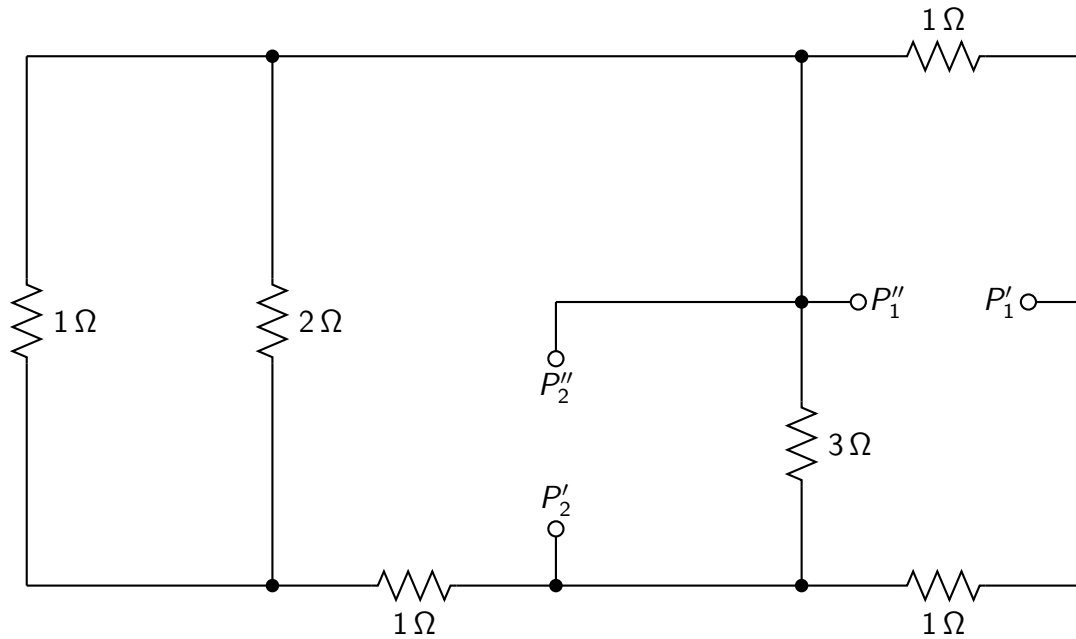


Problem: find the Resistance matrix of the two-port.



Solution

$$\mathbf{R} = \begin{pmatrix} \frac{29}{43} & \frac{15}{43} \\ \frac{15}{43} & \frac{30}{43} \end{pmatrix} \Omega$$