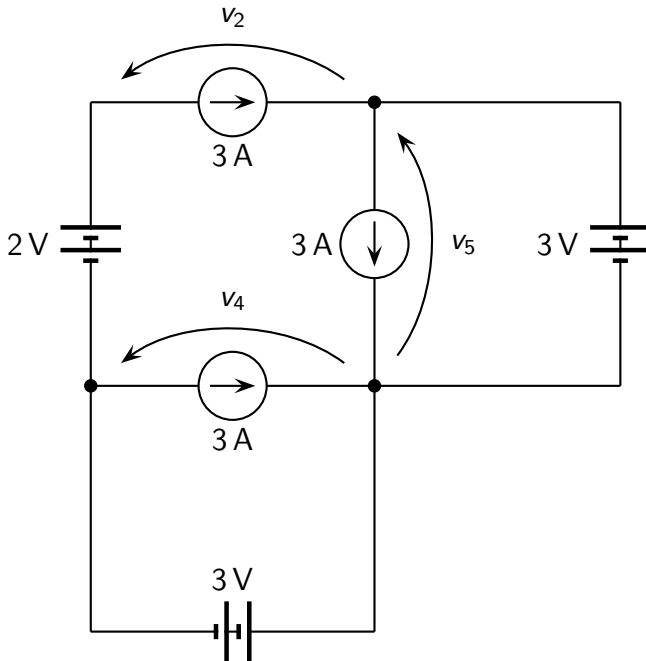


Problem: find v_2 , v_4 , v_5 .



Solution

$$v_2 = -4 \text{ V}$$

$$v_4 = -3 \text{ V}$$

$$v_5 = 3 \text{ V}$$

