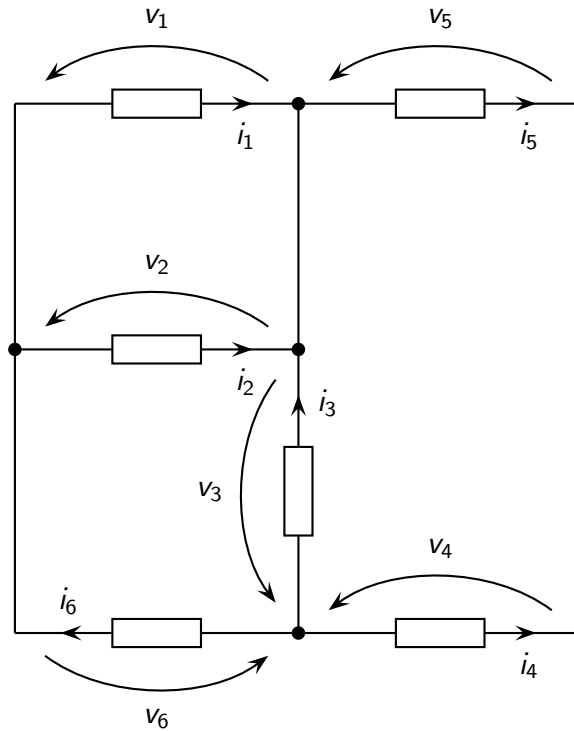


Problem: find v_2 , i_4 , i_5 .

Data: $i_1 = 1\text{ A}$, $i_2 = 3\text{ A}$, $i_3 = 3\text{ A}$, $v_4 = 1\text{ V}$, $v_5 = 2\text{ V}$, $v_6 = 3\text{ V}$



Solution

$$v_2 = -4 \text{ V}$$

$$i_4 = -7 \text{ A}$$

$$i_5 = 7 \text{ A}$$

