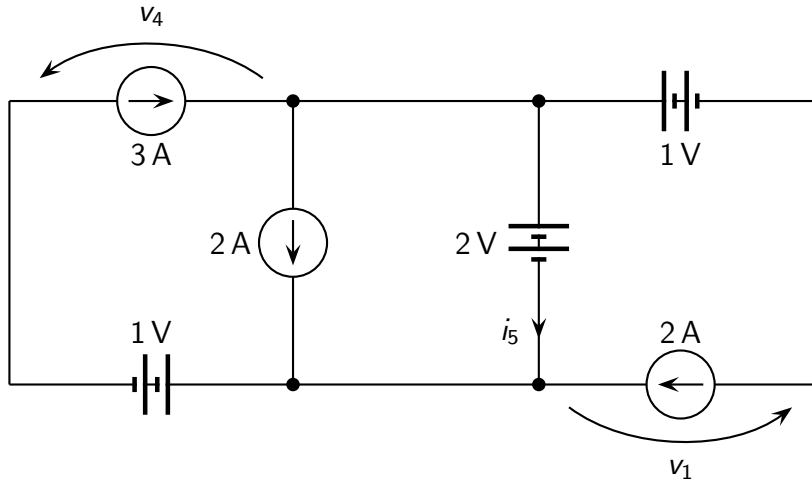


Problem: find v_1 , v_4 , i_5 .



Solution

$$v_1 = 1 \text{ V}$$

$$v_4 = -3 \text{ V}$$

$$i_5 = -1 \text{ A}$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).