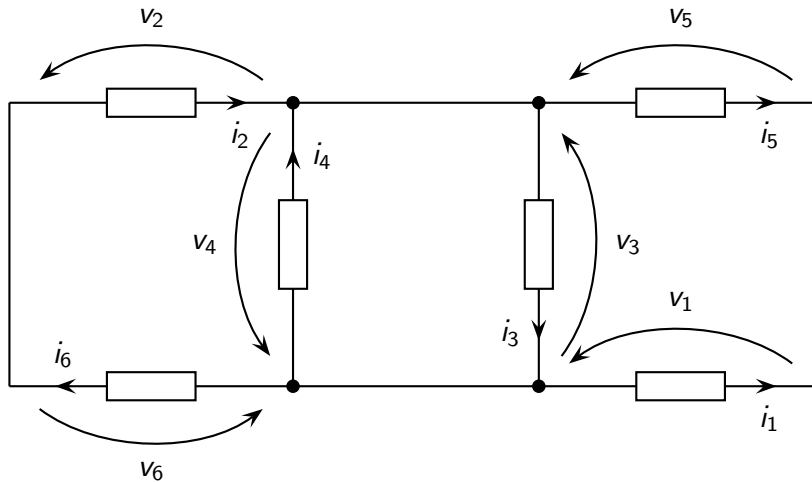


Problem: find v_1 , v_2 , v_3 .

Data: $v_4 = 3\text{ V}$, $v_5 = 3\text{ V}$, $v_6 = 1\text{ V}$



Solution

$$v_1 = 6\text{ V}$$

$$v_2 = 2\text{ V}$$

$$v_3 = -3\text{ V}$$



This work is licensed under a [Creative Commons Attribution-NonCommercial 4.0 International License](https://creativecommons.org/licenses/by-nc/4.0/).