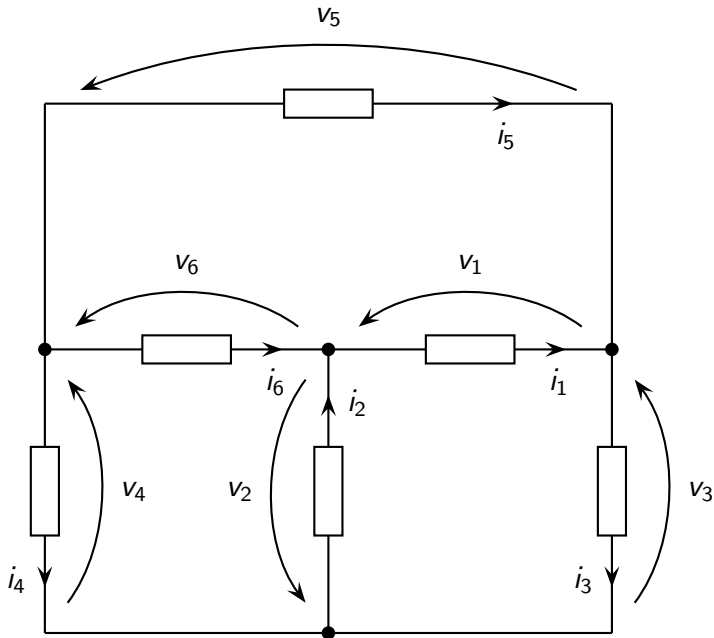


Problem: find v_1 , i_4 , v_6 .

Data: $i_1 = 1\text{ A}$, $v_2 = 3\text{ V}$, $i_3 = 1\text{ A}$, $v_4 = 1\text{ V}$, $v_5 = 2\text{ V}$, $i_6 = 2\text{ A}$



Solution

$$v_1 = -2 \text{ V}$$

$$i_4 = -2 \text{ A}$$

$$v_6 = 4 \text{ V}$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.