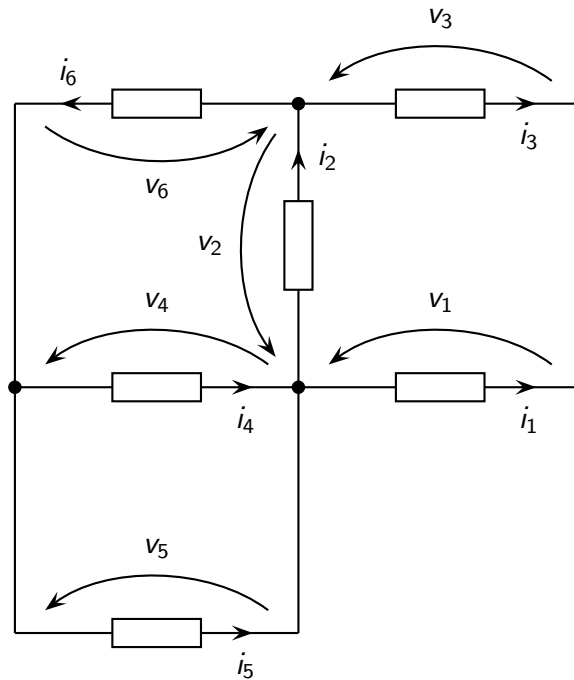


Problem: find v_1 , v_2 , i_3 .

Data: $i_1 = 1\text{ A}$, $i_2 = 3\text{ A}$, $v_3 = 3\text{ V}$, $v_4 = 3\text{ V}$, $i_5 = 2\text{ A}$, $v_6 = 3\text{ V}$



Solution

$$v_1 = -3 \text{ V}$$

$$v_2 = -6 \text{ V}$$

$$i_3 = -1 \text{ A}$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.