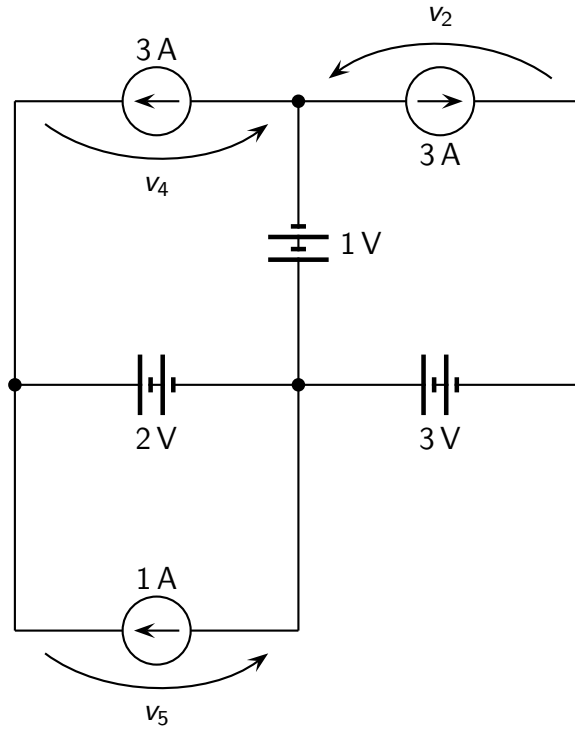


**Problem:** find  $v_2$ ,  $v_4$ ,  $v_5$ .



## Solution

$$v_2 = 2\text{ V}$$

$$v_4 = -3\text{ V}$$

$$v_5 = -2\text{ V}$$



This work is licensed under a Creative Commons Attribution-NonCommercial 4.0 International License.